

Content

1	REQUIREMENTS.....	3
2	Description with state graph.....	4
3	Pulse chart of the machine.....	5
4	RTL - the state machine.....	6


1 Description with state graph

License:

- **STATE_OPEN**: The door is open.
- **STATE_CLOSED**: The door is closed.
- **STATE_LOCKED**: The door is locked.
- **STATE_ERROR**: Error, the door is open but the lock button is pressed.

Transitions:

- From **STATE_OPEN** to **STATE_CLOSED**: When KEY0 is pressed.
- From **STATE_CLOSED** to **STATE_OPEN**: When KEY1 (open) is pressed.
- From **STATE_CLOSED** to **STATE_LOCKED**: When KEY2 (lock) is pressed.
- From **STATE_LOCKED** to **STATE_CLOSED**: When KEY3 (unlock) is pressed.
- From **STATE_OPEN** to **STATE_ERROR**: When KEY2 (lock) is pressed while the door is open.
- From **STATE_ERROR** to **STATE_OPEN**: When reset_n (reset) is activated.

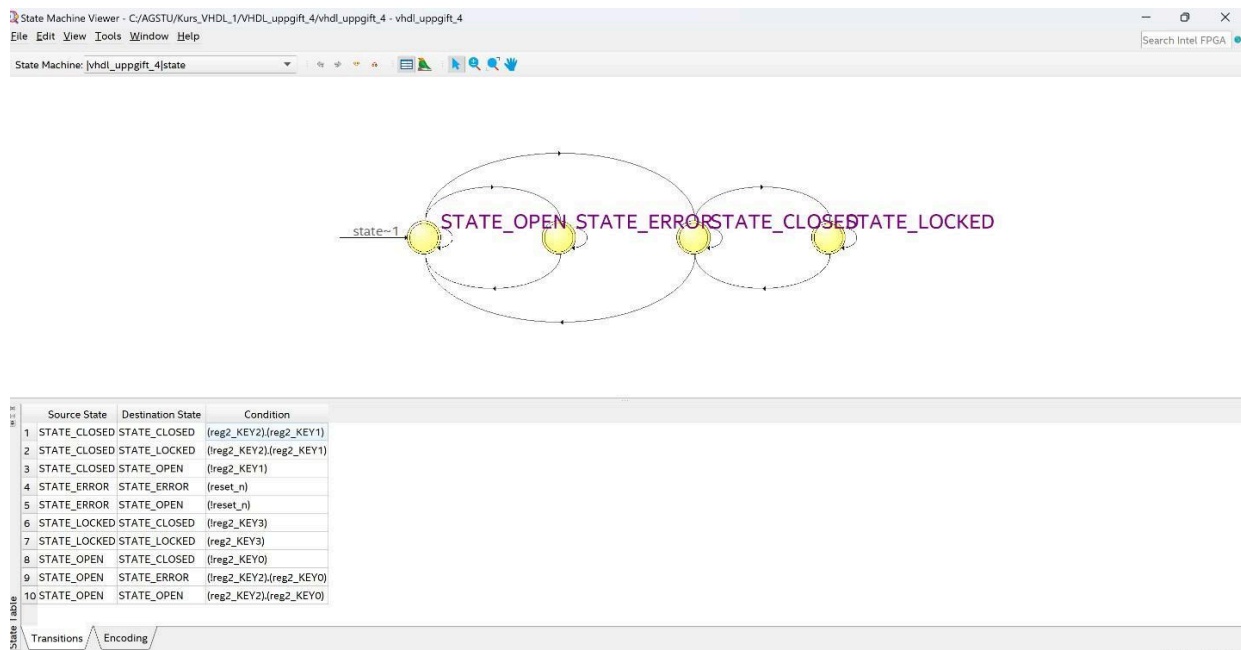


Name		STATE_ERROR	STATE_LOCKED	STATE_CLOSED	STATE_OPEN
1	STATE_OPEN	0	0	0	0
2	STATE_CLOSED	0	0	1	1
3	STATE_LOCKED	0	1	0	1
4	STATE_ERROR	1	0	0	1

State Table

Transitions

Encoding

2 Pulse chart of the machine

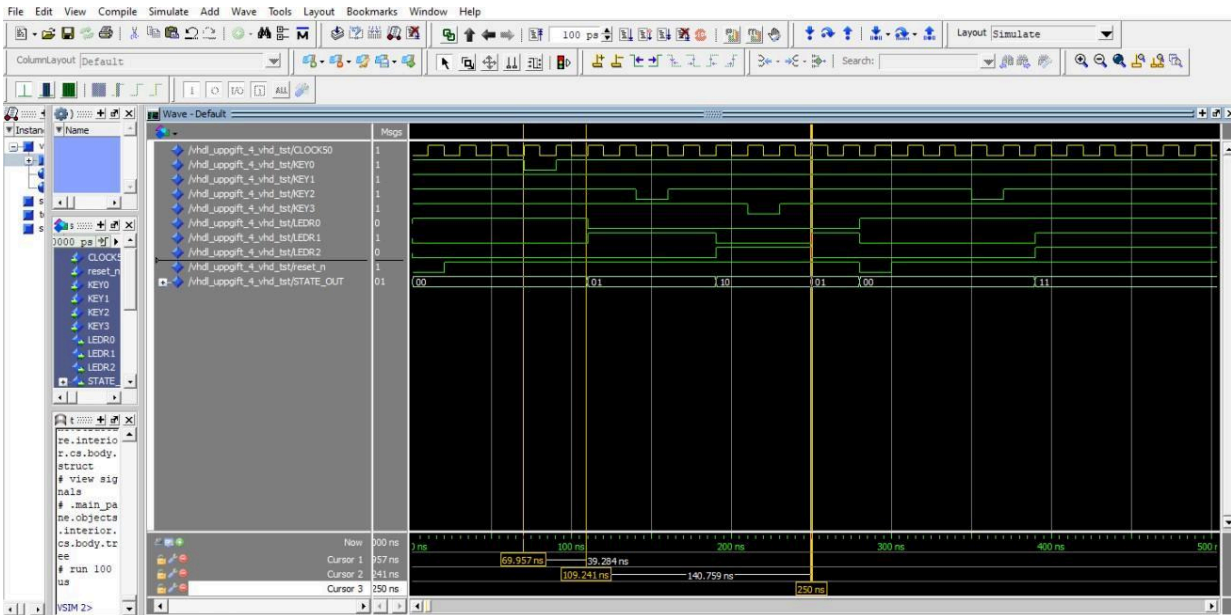

3 RTL – the state machine

1 Permit register:

state: Keeps current state.


next_state: Holds the next state.

2 State transition logic:

A process that takes in current conditions and input signals to set next_state.

3 Gates:

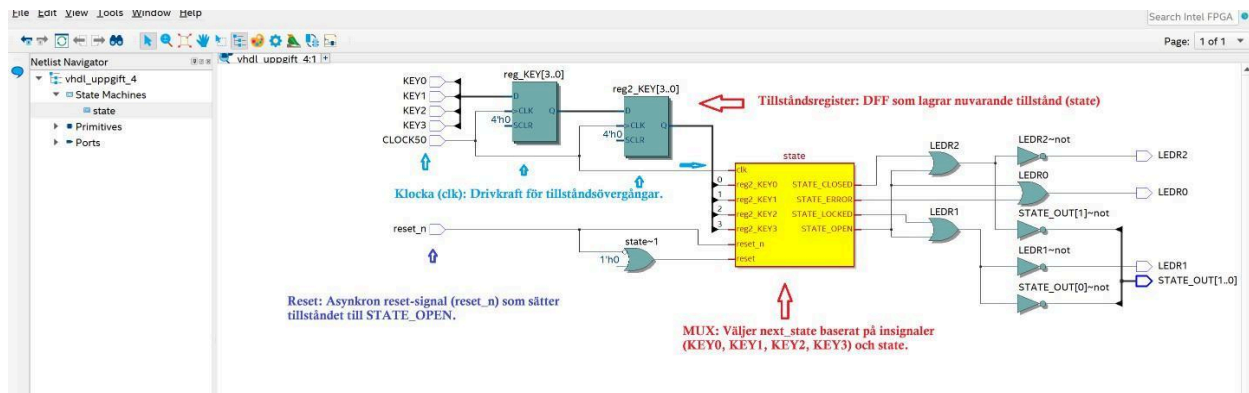Multiplexes (MUX) to select the next state based on the current state and keystrokes. D-flip-flops (DFF) to store the state.



Summary

The state machine for the door control with lock is defined by four states and transitions based on the user's input. The RTL representation uses DFF and MUX to manage state transitions and storage.